

# Hard ware assignment report

## AI22BTECH11015

Aishwarya Kunche

### COMPONENTS:

Components	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR GATE	7486	1
555 IC		1
Resistor	1K $\Omega$	1
Resistor	1M $\Omega$	1
Capacitor	100nF	1
Capacitor	10nF	1
Jumper Wires		20

### Description:

**Breadboard:** It is basically a plastic board with grid holes where holes are connected in a specific manner. This breadboard allows us to connect different components like resistors, capacitors, IC's..etc. Here, holes are arranged typically in a group of 5 called node. Holes in a row are electrically connected and in column are isolated.

**Seven Segment Display:** It is an output device which generates the numbers between 0 and 9. In our experiment it is used to display the generated random number.

**Decoder:** It acts as a bridge between the IC's and the output device *Display* which helps to convert the binary code into corresponding signals to display, to give the output.

**Two Flip Flops 7474:** These flip flops are used to create the shift registers, which is used to store and shift the data bits one by one.

**X-OR gate 7486:** It is used to give feedback connections between the flipflops in the shift register, enabling the shifting of data bits.



**555 timer:** It is used as a clock generator to provide a clock signal that controls the shifting of data in shift register.

**Resistors:** It is used in conjunction with 555 IC to set the timing and frequency of the clock signal.

**Capacitors:** It is used with 555 IC timer to stabilize the voltage and providing the timing control.
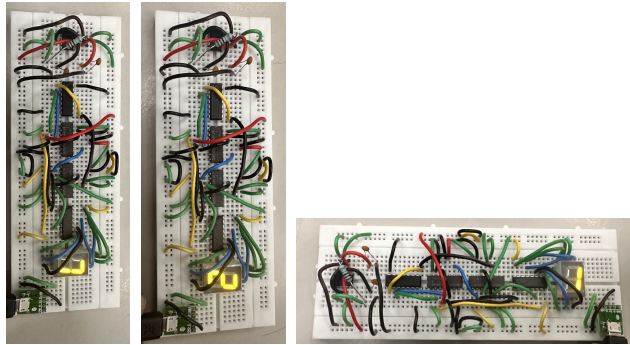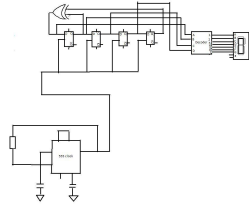
### PROCEDURE:

- First, we need to setup the 555 timer as shown in the above image in the breadboard.
- Next, we need to use the jumper wires to give the connection in the grids to all the IC's in the breadboard, just exactly how they are connected in the above figure.



- Connect the CLOCK output of the 555 timer circuit to CLOCK signal of the D-Flip Flops.
- Now make the circuit for shift registers using 4 D Flip Flops (by using two 7474 IC's) and one X-ORgate)(7486 IC).
- Connect the output of each D Flip flop to decoder IC (7447 IC), The pinout of 7447 IC.
- As per the pin out of IC 7474 [2, 12] pins of both IC's need to connected to the [7, 1, 2, 6] of decoder IC respectively.
- Make connections between the seven segment display and the 7447 IC.
- Additionally make connections like Vcc and GND to every IC as per the respective IC pinout for IC's 7474,7447,7486.

**CONCLUSION:** The experiment shows that shift registers can succesfully produce random variables. A random sequence can be convereted into a random variable with the correct probability distribution by carefully designing the shit register circuit and choosing the right feedback tap places.